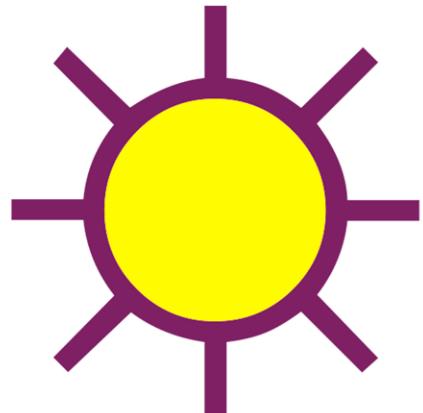


HOW TO MAKE A

# G☀GGAB☀T

I-G☀ggab☀t ine-njini esebenza ngamadla elanga, eqoqa amandla elanga ukuze ikhone ukusebenza.



Faka i-glue eshisayo emanqhineni, ukuze a n g a h l e p h u k i makwenzeka ugobisa ucingo.

ama-bhetri adinga ukuthamela ilanga ukuze athole amandla

MOTOR

SOLAR CELL

Ucingo olumnyama li-negative (-), kanti olubomvu li-positive (+)

CAPACITOR



Umugqha okwi-capacitor, kanye lomenze omufishane wocingo, izimpawu za-negative (-)

SOLAR CELL



Zama ukuthola ukuthi ubakhona yini umehluko mawusebenzia enye i-capacitor.

Makwenzeka imoto yakho inoku gq huma-gq huma, namathisela i-brush nge-glue emanzi. Uma uthola ukuthi i-moto yakho ayinankinga, zama ukuhlanganisa okusamzimba ngamasondo nocingo. Kubalulekile ukuqiniseka ukuthi i-robot yakho ikhone ukuhamba, ngakho qikelela ukuthi uyakha ngendlela ezokwenza kubelula ukuthi amalungu omzimba wayo alingane ukuze ingawi.


Amandla elanga awapheli. Masiwasebenzia, songa amandla nogesi wezinto eziFana namafutha, kanye namalahle, phezu kwalokho sisize imvelo.

OKUBALULEKILE: I- g☀ggab☀t yakho akumele ingene emgqhomeni ojwalekile, ilahle kwimiqghomo yadoti obizwa nge-E-waste.


⬇ Funda habanzi lapha ⬇

FREE SUNSHINE.ORG




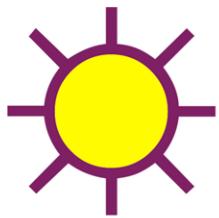

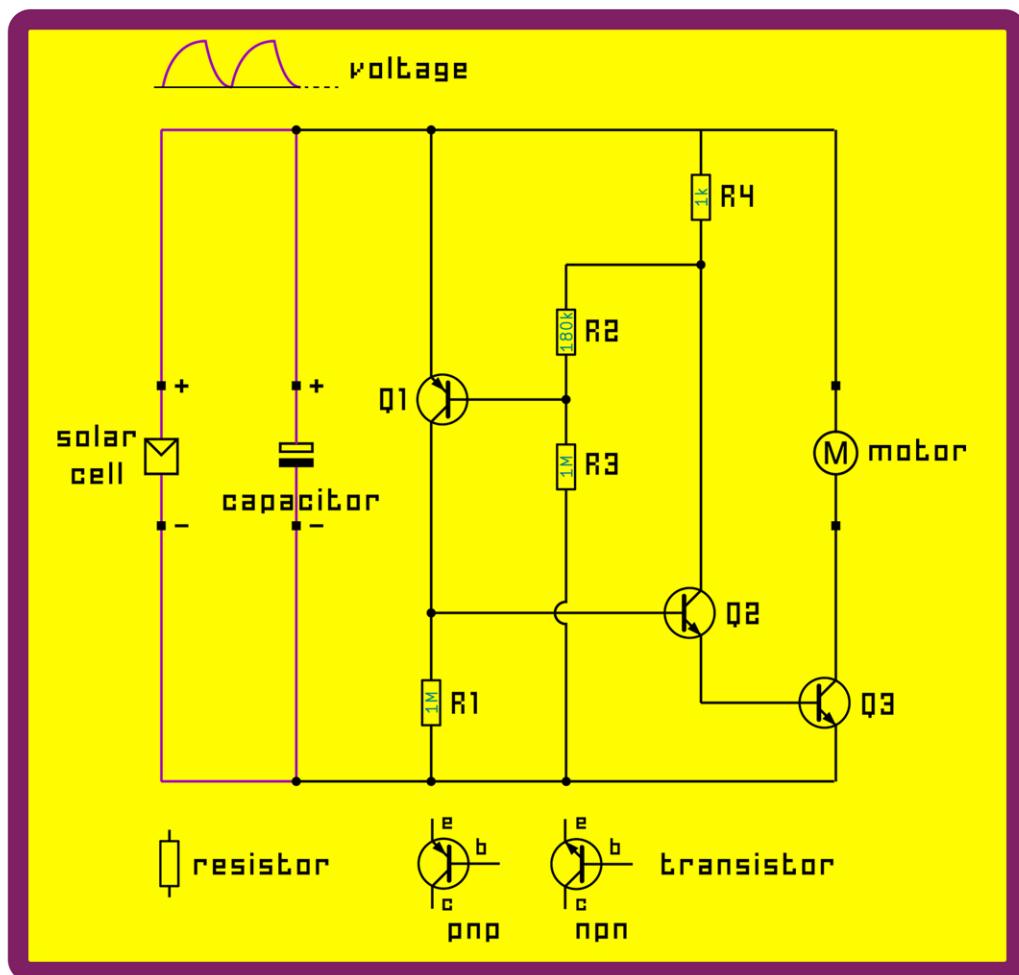I-gSOLARggabOT ine-solar cell, i-capacitor, i-control circuit (itholakala kucephe oluphuzi) kanye ne-moto. Isiphendula masondo inama-resistor amane (R1-R4), kanye nama-transistors (Q1-Q3).



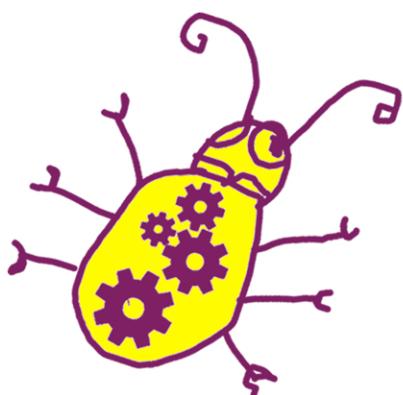isikhokha mandla siqoqa amandla avela elangeni, iwashintshe abe ugesi onama-volt amathathu. Lokhu kuphakela ama-capasitors ukuze okubizwa ngogesi welanga unyuke.



Kuthi lamandla angafika kuma-volt awu - 0.5V kwi-resistor yesisibili ama-transistors awale ukujikisa i-moto.

Ama-transistors ayeka ukuphaka ugesi makweliha ama-volt, iphinde iqale kabusha Futhi.